



Connecting Outdoor PIR's to your Z-Wave Network

Universal PIR's normally just have 3 wires (live, neutral and output). By utilising a Goap (Quibino) single relay, we can feed the PIR into the switch input on the Goap. After doing this we can see the PIR being triggered as a switch change on the Z-Wave gateway. By utilising this as a scene trigger, we can carry out any action including switching the same Goap relay to turn on an outside light or what have you. Below is an example of how this would be wired.

